

CSE 331/503 Computer Organization Homework 3 Report— ALU with Multiplication Design Hasan Mutlu — 1801042673

1. mult32.v Module

High Level State Machine:

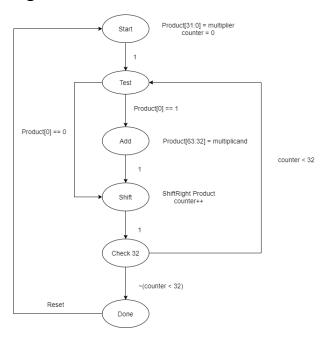

Finite State Machine:

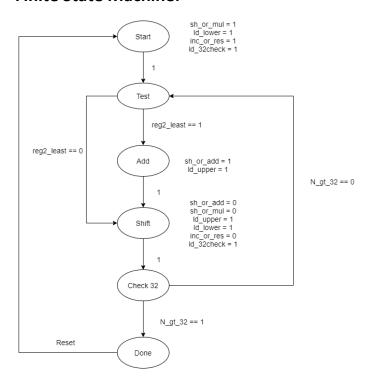

State Table:

State	Definition	R[2]	R[1]	R[0]
Start	Initialize multiplier to second register Initialize the counter	0	0	0
Test	Check least significant bit in product	0	0	1
Add	Add multiplicand to first register	0	1	0
Shift	Shift the product and save it Increment counter	0	1	1
check32	Check if counter reached 32	1	0	0
Done	Result is ready	1	0	1

States	R[2]	R[1]	R[0]	input	N[2]	N[1]	N[0]	Next State
Start	0	0	0	1	0	0	1	Test
Test	0	0	1	reg2_least	0	1	0	Add
	0	0	1	~reg2_least	0	1	1	Shift
Add	0	1	0	1	0	1	1	Shift
Shift	0	1	1	1	1	0	0	check32
check32	1	0	0	~N_gt_32	0	0	1	Test
	1	0	0	N_gt_32	1	0	1	Done
Done	1	0	1	Reset	0	0	0	Start
	1	0	1	~Reset	1	0	1	Done

N2 = R2'.R1.R0 + R2.R1'.R0'. N_gt_32 + R2.R1'.R0.Reset'

N1 = R2'.R1'.R0 + R2'.R1.R0'

N0 = R2'.R1'.R0' + R2'.R1'.R0. reg2_least' + R2'.R1.R0' + R2.R1'.R0' + R2.R1'.R0.Reset'

Sh_or_mul = R2'.R1'.R0'

Ld_lower = R2'.R1'.R0' + R2'.R1.R0


Ld_32check = R2'.R1'.R0' + R2'.R1.R0

Inc_or_res = R2'.R1'.R0'

Sh_or_add = R2'.R1.R0'


Ld_upper = R2'.R1.R0'+ R2'.R1.R0

Datapath:

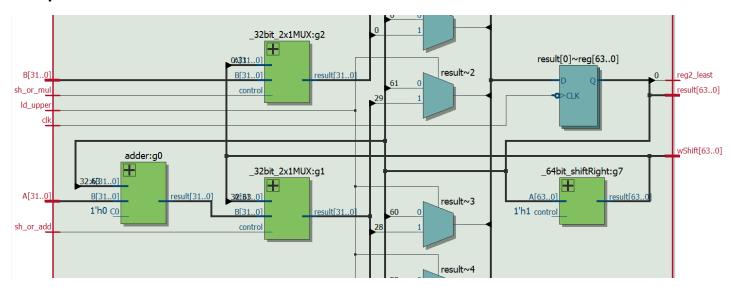

- *The muxes on the middle are load input or keep state selection of 64bit register.
- G2 Mux gets shift[31:0] and multiplier as data, sh or mul as control.
- G1 Mux gets shift[63:32] and addition result as data, sh_or_add as control.


ShiftRight's control is always 1.

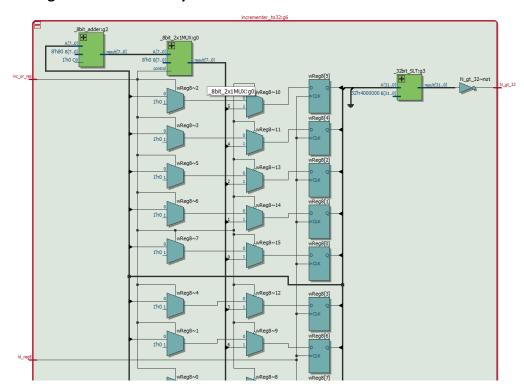

Datapath also incudes incrementer_to32 component. It is a counter up to 32.

It takes inc_or_res to increment or reset the counter. And Id_reg8 to load 8 bit register.

Testbench Result of mult32:

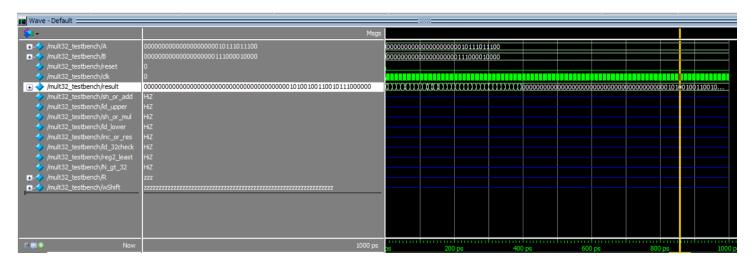


Convert Binary Value to Decimal Value




1500*3600 = 5400000


Controller:

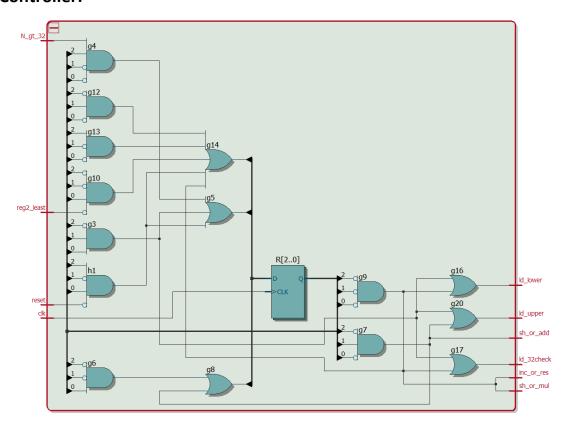

1. alu32.v Module

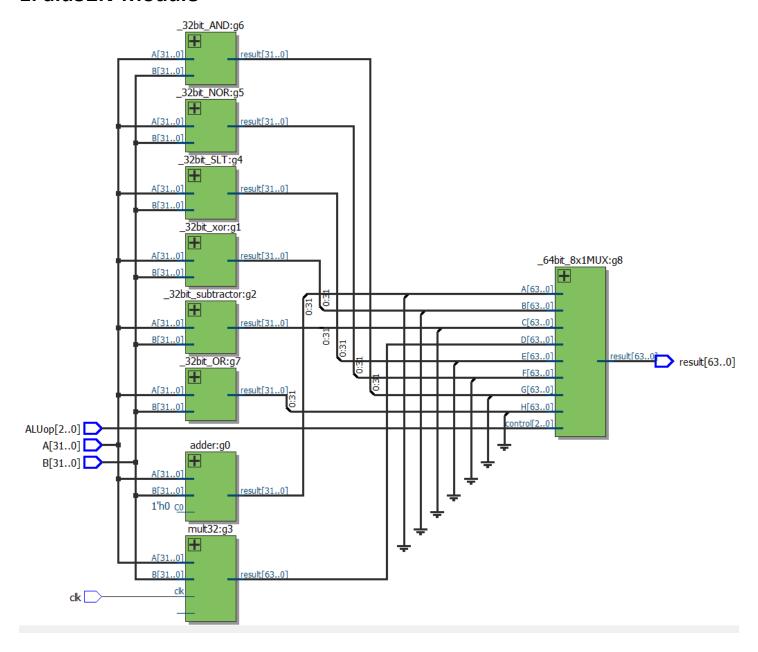

000.) Add Component: adder

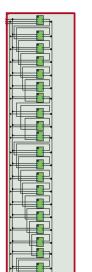

It consists of 32 full adders.

Testbench Results:



Convert Binary Value to Decimal Value



999999 + 11111111 = 2111110



Convert Binary Value to Decimal Value




55555 + 44444 = 99999


001.) XOR Component: _32bit_XOR


It consists of 32 XOR gates.

Testbench Results:

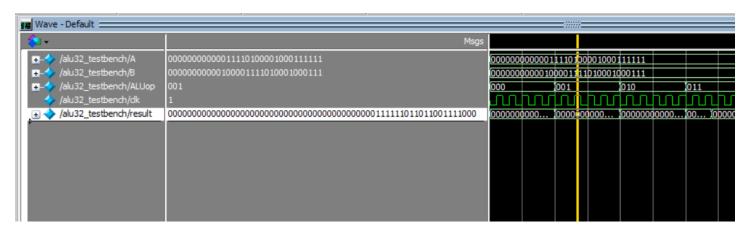


XOR Calculator

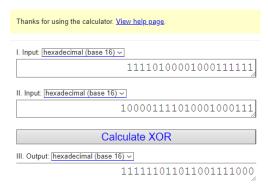


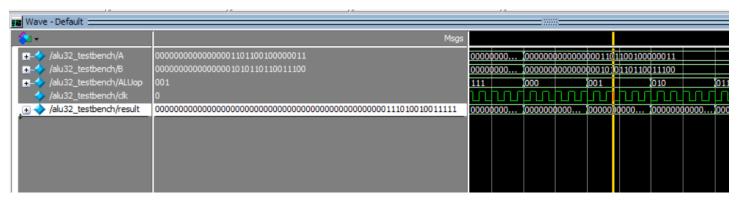


XOR Calculator

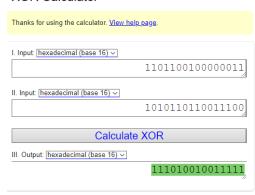

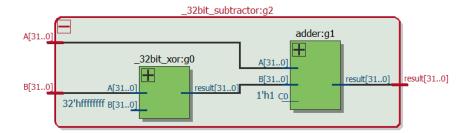010) Submission Component: _32bit_subtractor




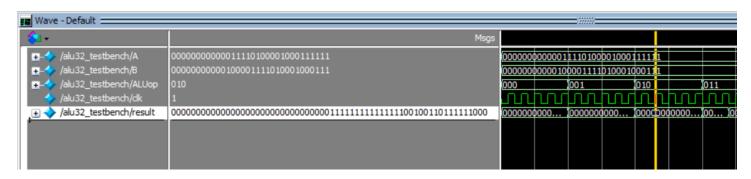It consists of one 32bit XOR block and one adder.






999999 - 1111111 = -111,112

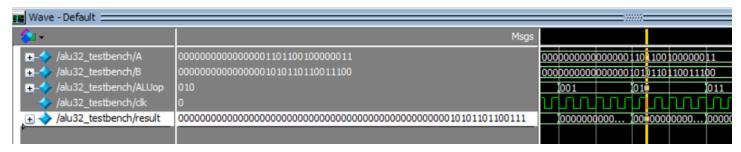


Convert Binary Value to Decimal Value




011) Multiplication Module: mult32

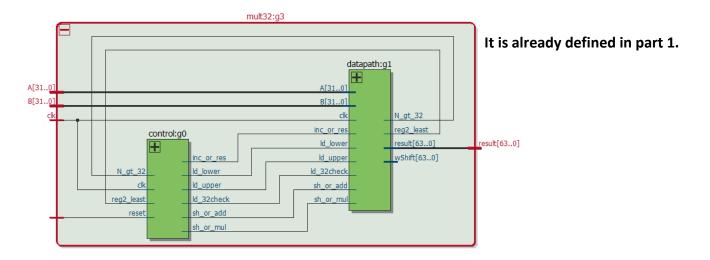

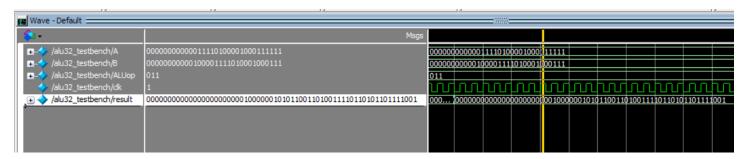

Convert Binary Value to Decimal Value

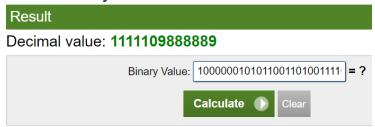



999999 * 1111111 = 1111109888889

→ Unfortunately, I couldn't reset the multiplier after first call, so there isn't a second testbench result in alu32_testbench.

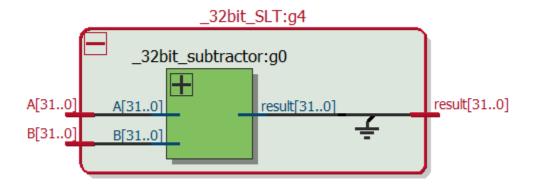100) Set on less than Component: _32bit_SLT

It consists of a 32 bit subtractor. Result's most significant bit is returned as result.



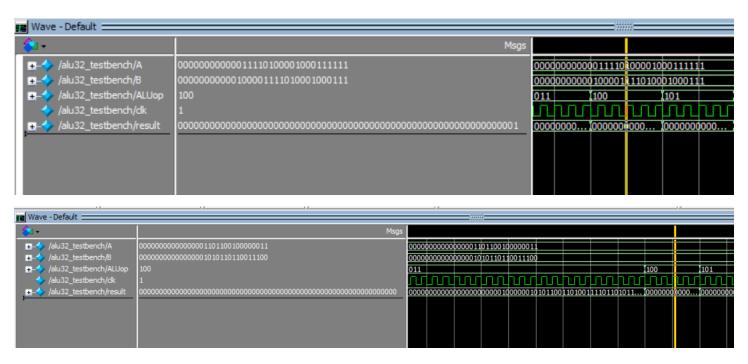


999999 < 1111111 == true

55555 < 44444 == false

Validity of the results are obvious.

101.) NOR Component: _32bit_NOR

It consists of 32 consecutive NOR gates.

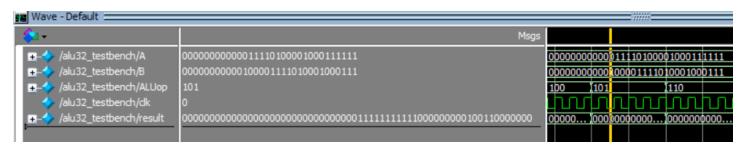


binary



11111111111000000000100110000000



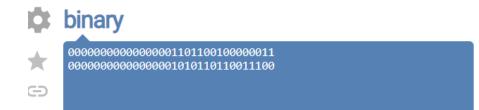




11111111111111110000001001100000

110) AND Component: _32bit_AND

It consists of 32 consecutive and gates.






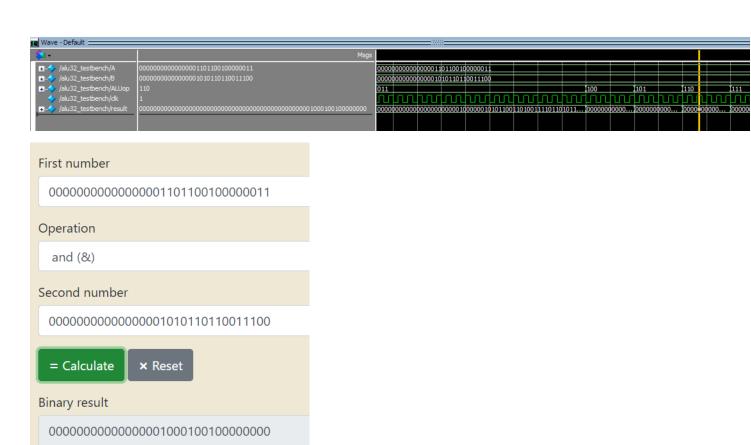


111.) OR Component: _32bit_OR

It consists of 32 consecutive or gates.

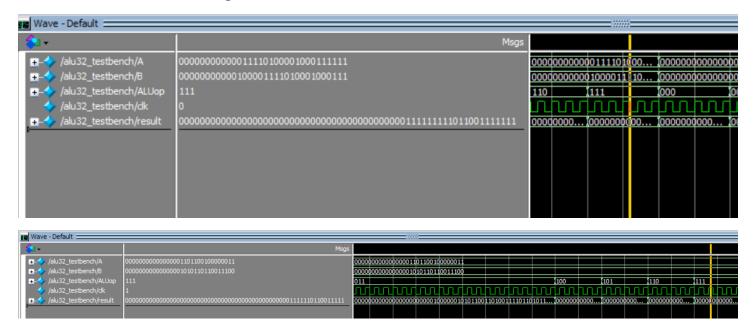

Helpful Components:

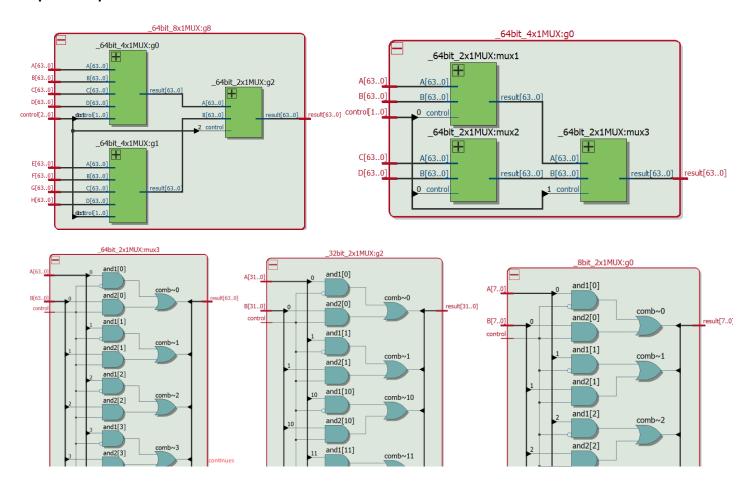

ShiftRight component includes 64 1bit 2x1 Muxes. Consecutive bit and current bit are connected to muxes and there is control. In this homework, this control input was always 1.

